

Q1

1) A four-bit binary number is represented as A3A2A1A0, where A3, A2, A1, and A0 represent the individual bits and A0 is equal to the LSB. Design a logic circuit using Verilog that will produce a HIGH output whenever the binary number is greater than 0010 and less than 1000.


- The design takes 1 input **A** (4-bits) and output **out** (1-bit)


```
//////////////////////////////// question_1 //////////////////////////////////  
  
module circuit_2 ( output out,  
                  input [3:0] A);  
    assign out = (A > 4'b0010 && A < 4'b1000) ? 1'b1 : 1'b0;  
  
endmodule
```



Q2

 
- 2) (a) Draw with your pen on a piece of paper the output waveform F for the circuit of Figure below.
(b) Repeat with the B input held LOW.
(c) Repeat with B held HIGH.



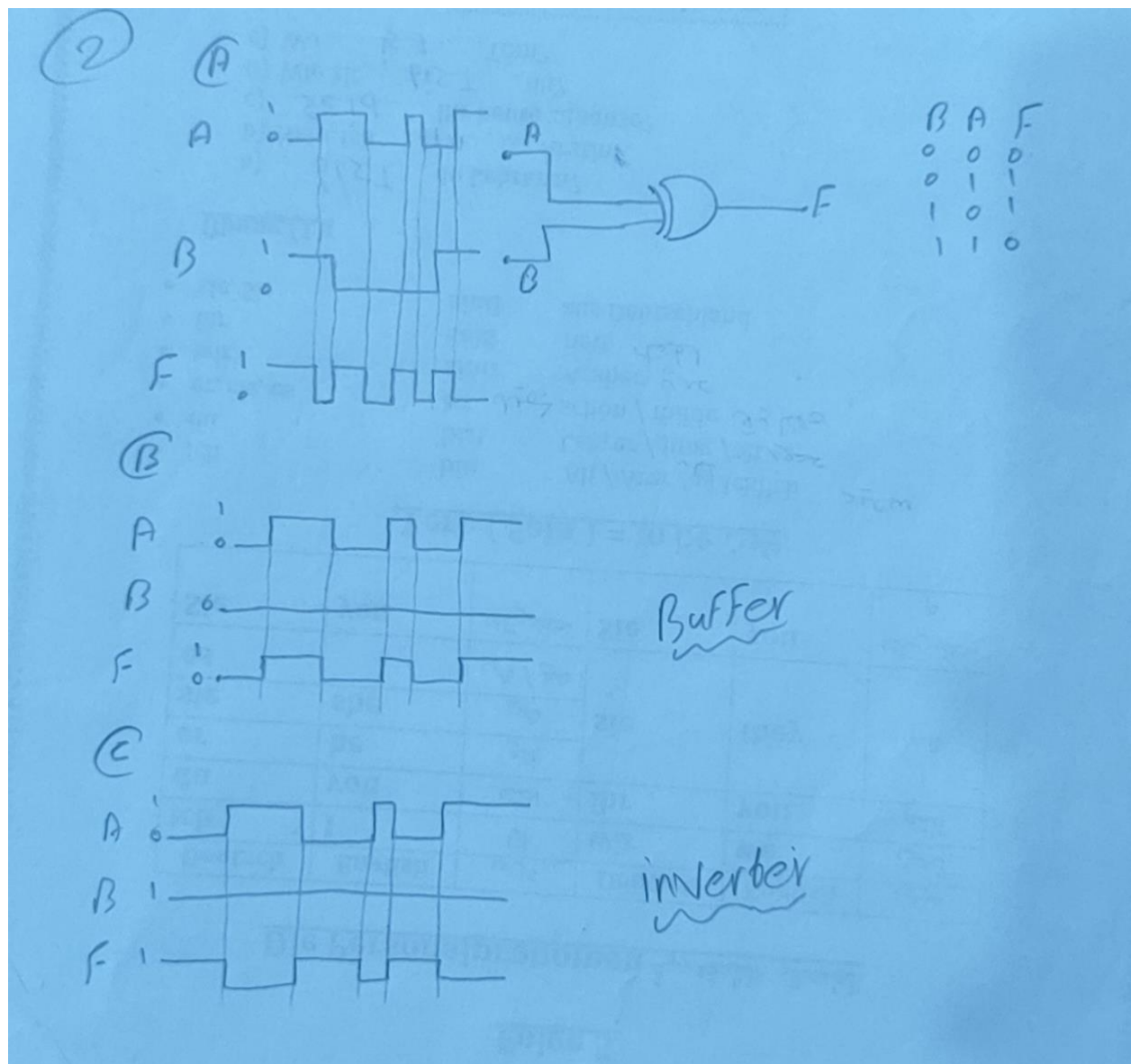


Q3

 3) Design the following circuit using Verilog and determine the input conditions needed to produce $F = 1$



```
//////////////////////////////// question_3 //////////////////////////////////
```

 
```
module circuit_3 ( output F,  
                  input A,B,C);  
  
    assign F = (A^B) & (B~^C) & (C);  
  
    /* F=1 when A=0 B=1 C=1 */  
  
endmodule
```



Q4

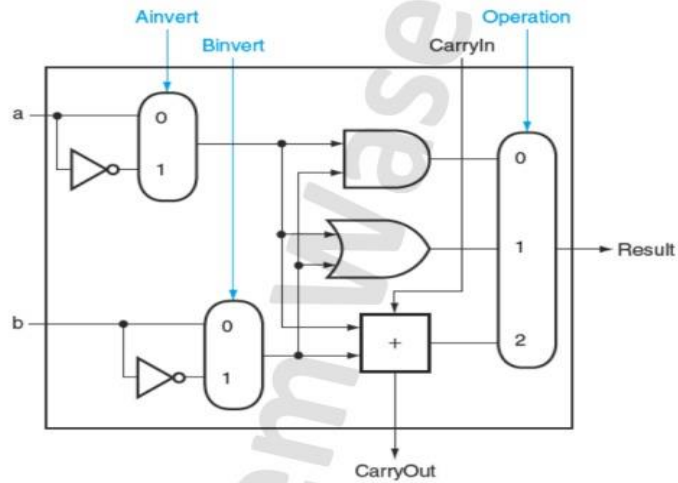4) Implement the following 1-bit ALU. If you are unfamiliar with the concept of an ALU, you can find more information by clicking [here](#). Use conditional operator for the multiplexers. For the 3-to-1 Mux, you can use the following format for the conditional operator.

assign <output_signal> = <condition1> ? <value1> : <condition2> ? <value2> : <default_value>;



Port Name	Type	Size	Description
A	Input	1 bit	Input a
B			Input b
<u>Ainvert</u>			Select signal for the multiplexer to select a or a complement
<u>Binvert</u>			Select signal for the multiplexer to select b or b complement
<u>CarryIn</u>			Carry in
Operation	Output	2 bits	Select signal for the multiplexer to drive the Result output
<u>CarryOut</u>		1 bit	Carry out
Result		1 bit	Output of the multiplexer

```
////////// question_4 //////////
```

```
module ALU ( output reg result,carry_out,
             input A,B,Ainvert,Binvert,carry_in,
             input [1:0] operation);
    wire w0,w1;
    MUX2_1 e (w0,A,~A,Ainvert);
    MUX2_1 f (w1,B,~B,Binvert);
    always @(*) begin
        case (operation)
            2'b00: result = w0&w1;
            2'b01: result = w0|w1;
            2'b10: {carry_out,result} = w0+w1+carry_in;
            default: result = 0;
        endcase
    end
endmodule
```

