 


- 1) Implement Data Latch with active low Clear. Implement a randomized testbench and check the output correctness from the waveform. Do not treat G input as a clock so add a delay (#1) after randomizing the inputs.



Input	Output
CLR, D, G	Q

**Truth Table**

CLR	G	D	Q
0	X	X	0
1	0	X	Q
1	1	D	D

assignment3.v

```
1  module d_latch ( output reg q,
2      input d,clr,g);
3      always @(*) begin
4          if (!clr)
5              q <= 0;
6          else if (g)
7              q <= d;
8      end
9
10 endmodule
11
12 module d_latch_ts ();
13     wire q;
14     reg d,clr,g;
15
16     d_latch w (q,d,clr,g);
17
18     initial begin
19         clr = 1; g = 0; d = 0; #1;
20         clr = 0; g = 1; d = 1; #1;
21         clr = 1; g = 1; d = 1; #1;
22         clr = 1; g = 0; d = 0; #1;
23         clr = 1; g = 1; d = 0; #1;
24         clr = 0; g = 1; d = 1; #1;
25         clr = 1; g = 1; d = 1; #1;
26         clr = 1; g = 1; d = 0; #1;
27         repeat (10) begin
28             d = $random;
29             g = $random;
30             #1;
31         end
32     end
33
34     initial begin
35         $monitor("q = %b, d = %b, clr = %b g = %b", q,d,clr,g);
36     end
37
38
39 endmodule
```

```

VSIM 23> run -all
# q = x, d = 0, clr = 1 g = 0
# q = 0, d = 1, clr = 0 g = 1
# q = 1, d = 1, clr = 1 g = 1
# q = 1, d = 0, clr = 1 g = 0
# q = 0, d = 0, clr = 1 g = 1
# q = 0, d = 1, clr = 0 g = 1
# q = 1, d = 1, clr = 1 g = 1
# q = 0, d = 0, clr = 1 g = 1
# q = 1, d = 1, clr = 1 g = 1
# q = 1, d = 1, clr = 1 g = 0
# q = 1, d = 1, clr = 1 g = 1
# q = 0, d = 0, clr = 1 g = 1
# q = 0, d = 1, clr = 1 g = 0
# q = 1, d = 1, clr = 1 g = 1

```

- A. Implement T-type (toggle) Flipflop with active low asynchronous reset (forces q to 0 and forces qbar to 1). T-Flipflop has input t, when t input is high the outputs toggle else the output values do not change.
  - Inputs: t, rstn, clk
  - Outputs: q, qbar
- B. Implement Asynchronous D Flip-Flop with Active low reset (forces q to 0 and forces qbar to 1).
  - Inputs: d, rstn, clk
  - Outputs: q, qbar
- C. Implement a parameterized asynchronous FlipFlop with Active low reset with the following specifications.
  - Inputs: d, rstn, clk
  - Outputs: q, qbar

- Parameter: FF\_TYPE that can take two valid values, DFF or TFF. Default value = "DFF". Design should act as DFF if FF\_TYPE = "DFF" and act as TFF if FF\_TYPE = "TFF". When FF\_TYPE equals "DFF", d input acts as the data input "d", and when FF\_TYPE equals "TFF", d input acts the toggle input "t".
- D. Test the above parameterized Design using 2 testbenches, testbench 1 that overrides the design with FF\_TYPE = "DFF" and the testbench 2 overrides parameter with FF\_TYPE = "TFF"
    - Testbench 1 should instantiate the design of part B. as a golden model to check for the output of the parameterized design with FF\_TYPE = "DFF"
      - Use a do file to run the simulation
    - Testbench 2 should instantiate the design of part A. as a golden model to check for the output of the parameterized design with FF\_TYPE = "TFF"
      - Use a do file to run the simulation

```

module t_flipflop ( output reg q,
                   output qbar,
                   inout t,clk,rstn);
    assign qbar = ~q;
    always @(posedge clk,negedge rstn) begin
        if (!rstn)
            q <= 0;
        else if (t)
            q <= ~q;
    end
endmodule

module d_flipflop ( output reg q,
                   output qbar,
                   input d,clk,rstn);
    assign qbar = ~q;
    always @(posedge clk,negedge rstn) begin
        if (!rstn)
            q <= 0;
        else
            q <= d;
    end
endmodule

module async_ff #(parameter [5*8-1:0] ff_type = "dff")
    (output reg q,
     output qbar,
     input d,clk,rstn);
    assign qbar = ~q;
    always @(posedge clk,negedge rstn) begin
        if (!rstn)
            q <= 0;
        else begin
            if (ff_type == "dff")
                q <= d;
            else if (ff_type == "tff")
                if (d)
                    q <= ~q;
        end
    end
endmodule

```

```

module async_ff_ts ();
    wire q,qbar;
    reg d,clk,rstn;
    async_ff #(.ff_type("dff")) tr (q,qbar,d,clk,rstn);
    initial begin
        clk = 0;
        forever #1 clk = ~clk;
    end
    initial begin
        d = 0;
        rstn = 0;
        @(negedge clk);
        rstn = 1;
        repeat (10) begin
            d = $random;
            @(negedge clk);
        end
    end

    end
    initial begin
        $monitor ("clk = %b d = %b rstn = %b q = %b qbar = %b", clk, d, rstn, q, qbar);
    end
end


endmodule

module async_ff_ts2 ();
    wire q,qbar;
    reg d,clk,rstn;
    async_ff #(.ff_type("tff")) tr (q,qbar,d,clk,rstn);
    initial begin
        clk = 0;
        forever #1 clk = ~clk;
    end
    initial begin
        d = 0;
        rstn = 0;
        @(negedge clk);
        rstn = 1;
        repeat (10) begin
            d = $random;
            @(negedge clk);
        end
    end

    end
    initial begin
        $monitor ("clk = %b d = %b rstn = %b q = %b qbar = %b", clk, d, rstn, q, qbar);
    end
end


endmodule

```

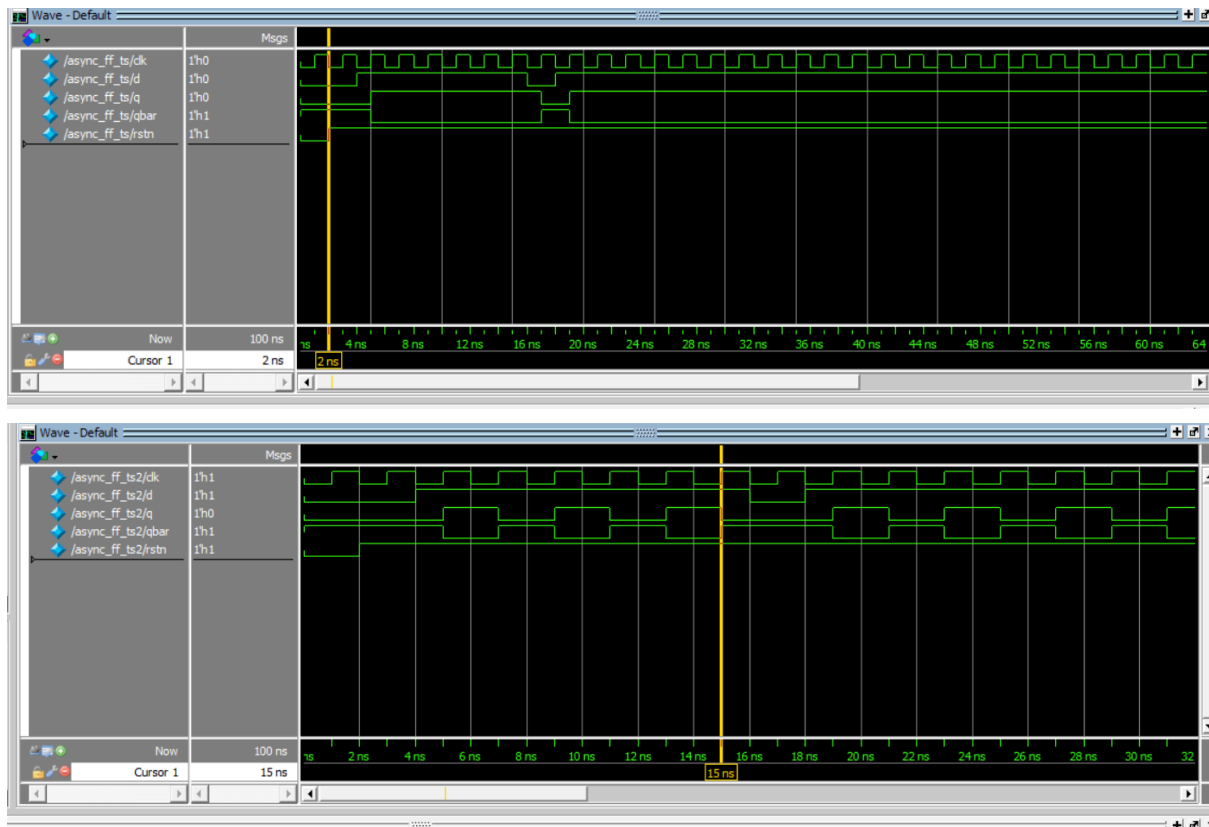

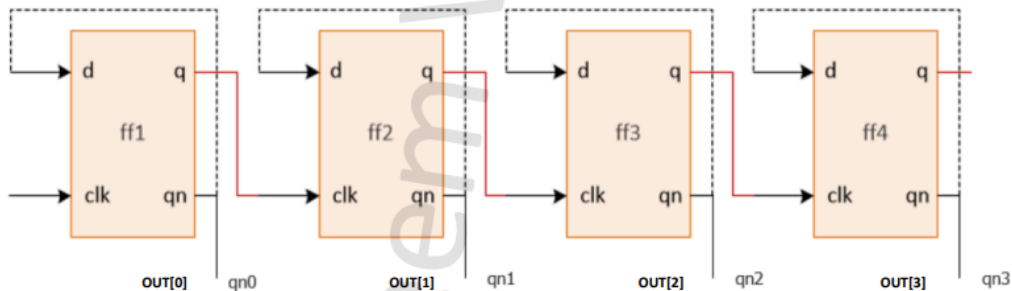- 3) Implement the 4-bit Ripple counter shown below using structural modelling (Instantiate the Dff from question 2 part B where the output is taken from the qn as shown below). Implement a randomized testbench and check the output correctness from the waveform.

- Inputs: clk, rstn;
- Outputs: [3:0] out;



```

module four_bit_counter ( output [3:0] out,
                          input clk,rstn);

    wire [3:0] q;
    d_flipflop q1 (q[0],out[0],out[0],clk,rstn);
    d_flipflop q2 (q[1],out[1],out[1],q[0],rstn);
    d_flipflop q3 (q[2],out[2],out[2],q[1],rstn);
    d_flipflop q4 (q[3],out[3],out[3],q[2],rstn);


endmodule

module four_bit_counter_ts ();
    wire [3:0] out;
    reg clk,rstn;

    four_bit_counter eq (out,clk,rstn);
    initial begin
        clk = 0;
        forever begin
            #1 clk = ~clk;
        end
    end
    initial begin
        rstn = 0;
        @(negedge clk);
        rstn = 1;
        repeat(100) @(negedge clk);
        $stop;
    end
    initial begin
        $monitor ("out = %b,clk = %b,rstn = %b",out,clk,rstn);
    end

endmodule

```

 


#### 4) Implement the following Parameterized Shift register

##### 1. Parameters

Name	Value	Description
LOAD_AVALUE	Integer > 0	Value loaded with aset is high
SHIFT_DIRECTION	"LEFT" or "RIGHT"	Direction of the shift register. Default = "LEFT"
LOAD_SVALUE	Integer > 0	Value loaded with sset is high with the rising clock edge
SHIFT_WIDTH	Integer > 0	Width of data[] and q[] ports

 Default value for LOAD\_AVALUE and LOAD\_SVALUE is 1. SHIFT\_WIDTH default value is 8.



##### 2. Ports

Name	Type	Description
sclr	Input	Synchronous clear input. If both sclr and sset are asserted, sclr is dominant.
sset		Synchronous set input that sets q[] output with the value specified by LOAD_SVALUE. If both sclr and sset are asserted, sclr is dominant.
shiftin		Serial shift data input
load		Synchronous parallel load. High: Load operation with data[], Low: Shift operation
data[]		Data input to the shift register. This port is SHIFT_WIDTH wide
clock		Clock Input
enable		Clock enable input
aclr	Output	Asynchronous clear input. If both aclr and aset are asserted, aclr is dominant.
aset		Asynchronous set input that sets q[] output with the value specified by LOAD_AVALUE. If both aclr and aset are asserted, aset is dominant.
shiftout		Serial Shift data output
q[]	Output	Data output from the shift register. This port is SHIFT_WIDTH wide

#### Notes:



```

module shift_register #( parameter LOAD_AVALUE =1,
                        parameter LOAD_SVALUE =1,
                        parameter SHIFT_WIDTH =8,
                        parameter SHIFT_DIRECTION = "LEFT")
( output reg [SHIFT_WIDTH-1:0] q,
  output reg shiftout,
  input [SHIFT_WIDTH-1:0] data,
  input sclr,sset,shiftin,load,clk,enable,aclr,aset);
always @(posedge clk , negedge aclr , negedge aset) begin
    if (aclr)
        q <= 0;
    else if (aset && !aclr)
        q <= LOAD_AVALUE;
    else if (!aclr && !aset) begin
        if (enable) begin
            if (sclr)
                q <= 0;
            else if (sset && !sclr)
                q <= LOAD_SVALUE;
            else begin
                if (load)
                    q <= data;
                else begin
                    if (SHIFT_DIRECTION == "LEFT") begin
                        shiftout <= q [SHIFT_WIDTH-1];
                        q <= {q[SHIFT_WIDTH-2:0],shiftin};
                    end
                    else if (SHIFT_DIRECTION == "RIGHT") begin
                        shiftout <= q [0];
                        q <= {shiftin,q[SHIFT_WIDTH-1:1]};
                    end
                end
            end
        end
    end
end
end
end
end
endmodule

```

```

module shift_register_ts ();
    parameter LOAD_AVALUE_TS = 2;
    parameter LOAD_SVALUE_TS = 4;
    parameter SHIFT_WIDTH_TS = 8;
    parameter SHIFT_DIRECTION_TS = "LEFT";
    wire [SHIFT_WIDTH_TS-1:0] q;
    reg [SHIFT_WIDTH_TS-1:0] q_expected;
    wire shiftout;
    reg [SHIFT_WIDTH_TS-1:0] data;
    reg sclr,sset,shiftin,load,clk,enable,aclr,aset;
    shift_register # (.LOAD_AVALUE(LOAD_AVALUE_TS),.LOAD_SVALUE(LOAD_SVALUE_TS),.SHIFT_WIDTH(SHIFT_WIDTH_TS),.SHIFT_DIRECTION(SHIFT_DIRECTION_TS))
        r (q,shiftout,data,sclr,sset,shiftin,load,clk,enable,aclr,aset);

    initial begin
        clk = 0;
        forever #1 clk = ~clk;
    end
    initial begin
        aclr = 1;
        aset = 1;
        repeat (10) begin
            data = $random;
            if (aclr)
                q_expected = 0;
            else begin
                if (aset)
                    q_expected = LOAD_AVALUE_TS;
            end
        end
        @(negedge clk);
    end

    aclr = 0;
    aset = 1;
    repeat (10) begin
        data = $random;
        if (aclr)
            q_expected = 0;
        else begin
            if (aset)
                q_expected = LOAD_AVALUE_TS;
        end
    end
    @(negedge clk);
end

```

```

        enable = 1;
        aset = 0;
        aclr = 0;
        sclr = 1;
        sset = 1;
        repeat (10) begin
            data = $random;
            if (!aset && !aclr)
                if (sclr)
                    q_expected = 0;
                else begin
                    if (sset)
                        q_expected = LOAD_SVALUE_TS;
                end
        end
        @(negedge clk);
    end

    aset = 0;
    aclr = 0;
    sclr = 0;
    sset = 1;
    repeat (10) begin
        data = $random;
        if (!aset && !aclr)
            if (sclr)
                q_expected = 0;
            else begin
                if (sset)
                    q_expected = LOAD_SVALUE_TS;
            end
        end
    end
    @(negedge clk);
end


```

```


    aclr = 0;
    aset = 0;
    sclr = 0;
    sset = 0;
    load = 1;
    repeat (10) begin
        data = $random;
        if (load) begin
            q_expected = data;
            @(negedge clk);
        end
    end

    aclr = 0;
    aset = 0;
    sclr = 0;
    sset = 0;
    load = 0;
    repeat (10) begin
        shiftin = $random;
        @(negedge clk);
    end
    $$stop;
end
initial begin
    $monitor("aclr=%b aset=%b sclr=%b sset=%b clk=%b load=%b shiftin=%b data=%b q=%b shiftout=%b q_expected=%b",aclr,aset,sclr,sset,clk,load,shiftin,data,q,shiftout,q_expected);
end
endmodule

```

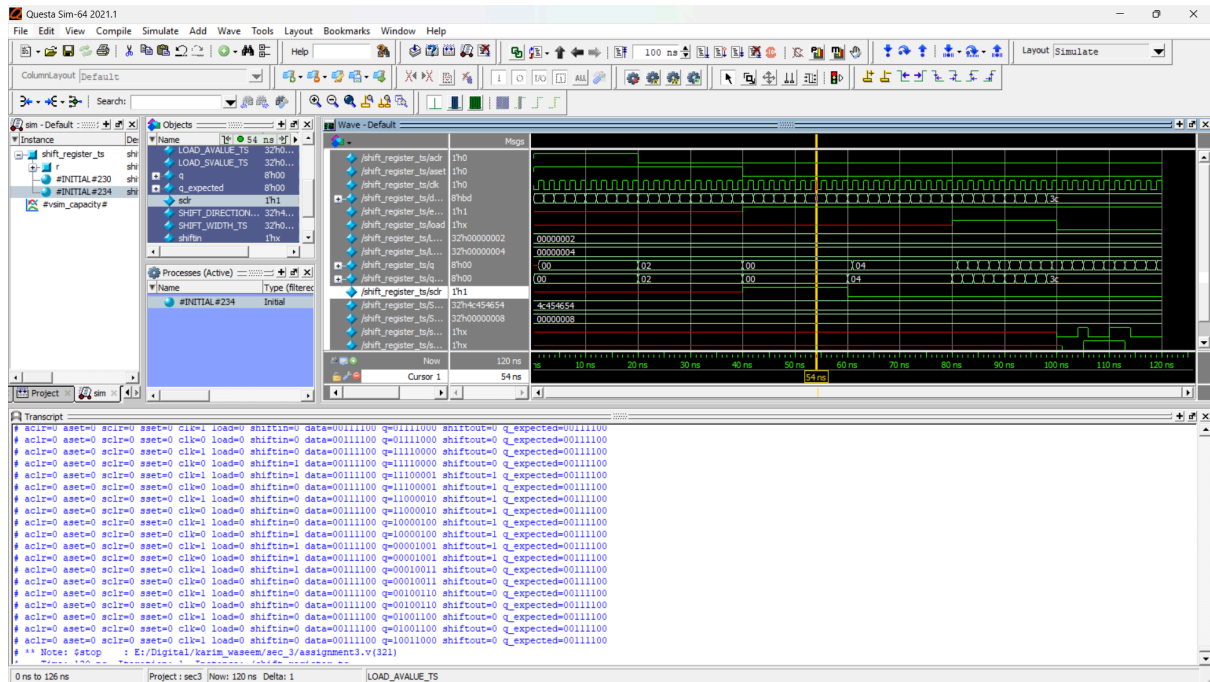

 - 5) Implement the following SLE (sequential logic element). This design will act as flipflop or latch based on the LAT signal as demonstrated in the truth table.



Input		Output
Name	Function	Q
D	Data	
CLK	Clock	
EN	Enable	
ALn	Asynchronous Load (Active Low)	
ADn*	Asynchronous Data (Active Low)	
SLn	Synchronous Load (Active Low)	
SD*	Synchronous Data	
LAT*	Latch Enable	

**Truth Table**

ALn	ADn	LAT	CLK	EN	SLn	SD	D	Q <sub>n+1</sub>
0	ADn	X	X	X	X	X	X	IADn
1	X	0	Not rising	X	X	X	X	Qn
1	X	0	↑	0	X	X	X	Qn
1	X	0	↑	1	0	SD	X	SD
1	X	0	↑	1	1	X	D	D
1	X	1	0	X	X	X	X	Qn
1	X	1	1	0	X	X	X	Qn
1	X	1	1	1	0	SD	X	SD
1	X	1	1	1	1	X	D	D

Testbench should start with activating ALn then deactivating it. Then for simplicity we keep the LAT to 0 and in a repeat block randomize all inputs. Then drive LAT to 1 and in a repeat block randomize all inputs. Check the functionality correctness of each input from the waveform.

```

module sle ( output q,
             input d,clk,en,aln,adn,sln,sd,lat);
reg q_flipflop,q_latch;
assign q = (lat) ? q_latch : q_flipflop;

always @(posedge clk , negedge aln , negedge adn) begin
    if (!aln)
        q_flipflop <= ~adn;
    else begin
        if (sln)
            q_flipflop <= d;
        else if (en)
            q_flipflop <= sd;
    end
end

always @(*) begin
    if (!aln)
        q_latch <= ~adn;
    else begin
        if (sln)
            q_latch <= d;
        else if (en)
            q_latch <= sd;
    end
end

endmodule

```

```

module sle_ts ();
  wire q;
  reg d,clk,en,aln,adn,sln,sd,lat;
  sle k (q,d,clk,en,aln,adn,sln,sd,lat);

  initial begin
    clk = 0;
    forever #1 clk = ~clk;
  end

  initial begin
    lat = 0;
    aln = 0;
    adn = 0;
    @(negedge clk);
    aln = 1;
    en = 1;
    repeat (5) begin
      d = $random;
      sd = $random;
      @(negedge clk);
      sln = 1;
      repeat (5) begin
        d = $random;
      end
    end
    lat = 1;
    aln = 0;
    adn = 0;
    sln = 0;
    @(negedge clk);
    aln = 1;
    en = 1;
    repeat (5) begin
      d = $random;
      sd = $random;
      @(negedge clk);
      sln = 1;
      repeat (5) begin
        d = $random;
      end
    end
    lat = 0;
    aln = 0;
    adn = 0;
    sln = 0;
    $stop;
  end

end

initial begin
  $monitor ("lat=%b clk=%b en=%b aln=%b adn=%b sln=%b sd=%b d=%b q=%b",lat,clk,en,aln,adn,sln,sd,d,q);
end

endmodule

```

