


Sheet 1

Q1-The exclusive-OR circuit of fig has gates with a delay of 3ns for an inverter, a 6ns for delay for an AND gate, and a 8ns for an OR gate. The input of the circuit goes from $xy=00$ to $xy=01$.

- (a) Determine the signals at the output of each gate from $t=0$ to $t=50\text{ns}$.
- (b) Write a Verilog gate-level description of the circuit, including the delays.
- (c) Write a stimulus module and simulate the circuit to verify the answer in part (a).

ANS

(a) Block diagram:-

 


Initially when $xy=00$, $W1=W2=1$, $W3=W4=0$, and $F=0$.

$xy=00 \rightarrow xy=11$:-

After 3ns from change $\rightarrow W1=0$, and $W2=1$.

After 6ns from change $\rightarrow W3=0$, and $W4=1$.

After 8ns from change $\rightarrow F=1$.

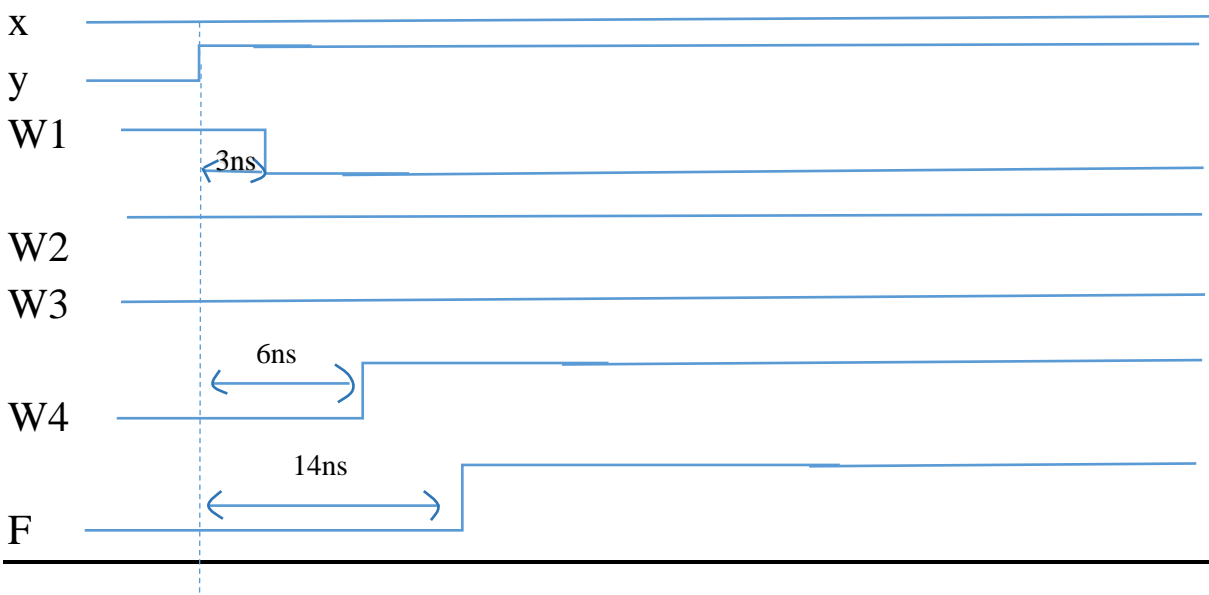


(b&c) Code:-

```
`timescale 1ns/1ps
module x_or_gate (output F,input X,Y);
wire W1,W2,W3,W4;
not #3 (W1,Y);
not #3 (W2,X);
and #6 (W3,X,W1);
and #6 (W4,Y,W2);
or #8 (F,W3,W4);
endmodule

module tb_x_or_gate ();
reg X,Y;
wire F;
x_or_gate tb(F,X,Y);
initial
begin
X=0;
Y=0;
#20 Y=1;
end
endmodule
```

Simulation:-

 

Q2-Using continues assignment,write a Verilog description of the circuit specified by the following Boolean functions:

$$\text{Out}_1 = (A+B')C'(C+D)$$

$$\text{Out}_2 = (C'D+BCD+CD')(A'+B)$$

$$\text{Out}_3 = (AB+C)D+B'C$$

ANS

Code:-


```
module circuit_3 (output Out_1,Out_2,Out_3,input A,B,C,D);
wire not_A,not_B,not_C,not_D;
assign not_A=~A;
assign not_B=~B;
assign not_C=~C;
assign not_D=~D;
assign Out_1 = (A|not_B)&not_C&(C|D);
assign Out_2 = ((not_C&D)|(B&C&D)|(C&not_D))&(not_A|B);
assign Out_3 = ((A&B|C)&D)|(not_B&C);
endmodule
`timescale 1ns/1ps
```

```

module tb_circuit_3 ();
reg A,B,C,D;
wire Out_1,Out_2,Out_3;
integer i;
circuit_3 tb (Out_1,Out_2,Out_3,A,B,C,D);
initial
begin
A=0;
B=0;
C=0;
D=0;
for (i=0;i<17;i=i+1)
#5 {A,B,C,D}={A,B,C,D}+1;
End
endmodule

```

Simulation:-

 

Q3-Find the syntax errors in the following declarations (note that names for primitive gates are optional):

```

module Exmpl-3(A,B,C,D,F)           //line 1
Inputs      A,B,C,Output D,F,      //line 2
output      B                      //line 3
and         g1(A,B,D);             //line 4
not         (D,A,C),               //line 5
OR          (F,B,C);               //line 6
endmodule;                          //line 7

```

ANS

Line 1: (-) not allowed to be in the module name , So use (_) instead of (-) , there is (;) required after).

Line 2: input not inputs , must be output not Output and there is required (;) after C, There is (;) required after F.

Line 3: B cant be declared as input and output.

Line 4: A cant be output because it's declared as input in port list,D cant be input because it's declared as output in port list.

Line 5: too many ports entire of not gate,there is (;) required afer).

Line 6: OR must be or.

Line 7: no (;) after endmodule.

So) **The code after editing should be:-**

```

module Exmpl_3(A,B,C,D,F);
input      A,B,C;
output     D,F;
and        g1(D,A,B);
not        (D,A ( /*or C*/))

```

Or
endmodule (F,B,C);

Q4-A majority logic function is a Boolean function that is equal to 1 if the majority of the variables are equal to 1, equal to 0 otherwise.

(a) Write a truth table for a four-bit majority function.

(b) Write a Verilog user defined primitive for a four-bit majority function.

ANS

(a) Truth table:-

A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

(b) Code:-

```
primitive maj_UDP (output F,input A,B,C,D);  
table  
0 0 0 0 : 0;  
0 0 0 1 : 0;  
0 0 1 0 : 0;  
0 0 1 1 : 0;  
0 1 0 0 : 0;  
0 1 0 1 : 0;  
0 1 1 0 : 0;  
0 1 1 1 : 1;  
1 0 0 0 : 0;  
1 0 0 1 : 0;  
1 0 1 0 : 0;  
1 0 1 1 : 1;  
1 1 0 0 : 0;  
1 1 0 1 : 1;  
1 1 1 0 : 1;  
1 1 1 1 : 1;
```

```


endtable
endprimitive

`timescale 1ns/1ps


module tb_maj_4_bit ();
reg A,B,C,D;
wire F;
integer i;
maj_UDP M(F,A,B,C,D);
initial
begin
A=0;
B=0;
C=0;
D=0;
for (i=1;i<17;i=i+1)
#5 {A,B,C,D}={A,B,C,D}+1;
end
endmodule

```

(c) Simulation:-

 


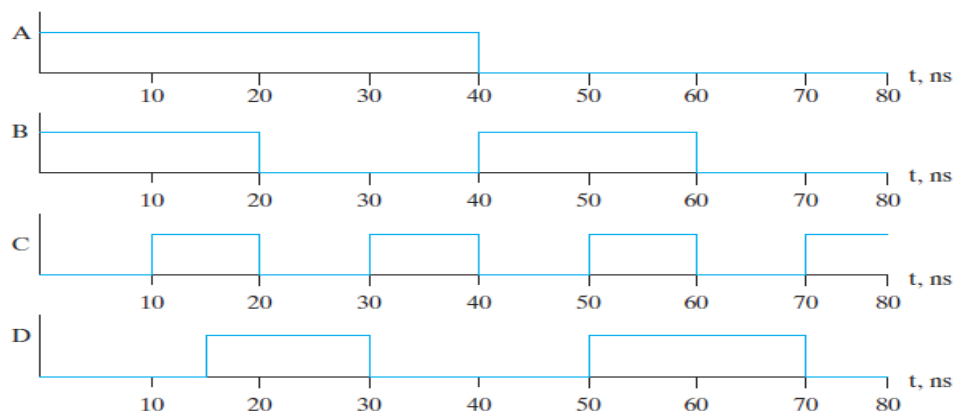Q5-Simulate the behaviour of circuit_with_UDP_02467, using the stimulus waveforms shown in fig.



ANS

(a) Block diagram:-

 

(b) Code:-

```
primitive UDP_02467 (output E,input A,B,C);
```

```
table
```

```
0 0 0 : 1;
```

```
0 0 1 : 0;
```

```
0 1 0 : 1;
```

```
0 1 1 : 0;
```

```
1 0 0 : 1;
```

```
1 0 1 : 0;
```

```
1 1 0 : 1;
```

```
1 1 1 : 1;
```

```
endtable
```

```
endprimitive
```

```
module circuit_UDP_02467 (output E,F,input A,B,C,D);
```

```
UDP_02467 DP (E,A,B,C);
```

```
and (F,E,D);
```

```
endmodule
```

```
`timescale 1ns/1ps
```

```
module tb_UDP_02467 ();
```

```
reg A,B,C,D;
```

```
wire E,F;
```

```
circuit_UDP_02467 UD (E,F,A,B,C,D);
```

```
initial
```

```
begin
```

