


abdalrahman taha Assignment\_1

Q1

Design the following circuits with Verilog using assign statements

 1)

- The design has 7 inputs and 2 outputs
- Use assign statements to design the following




```
//////////////// MUX2_1 //////////////////
module MUX2_1 ( output I,
                input A0,A1,sel);
    assign I = (sel ==0) ? A0 : A1;
endmodule

//////////////// question_1 //////////////////

module circuit_1 ( output out,out_bar,
                   input A,B,C,D,E,F,sel);

     wire w0,w1;
    and (w0,A,B,C);
    xnor (w1,D,E,F);
    MUX2_1 q0 (out,w0,w1,sel);
    not (out_bar,out);
endmodule
```



Q2


2) Implement 4-bit adder using addition operator and assign statement

- The design takes 2 inputs (A, B) and the summation is assigned to output (C) ignoring the carry

```

//////////////// question_2 //////////////////
module adder ( output [3:0] c,
               input [3:0] A,B);
    assign c = A + B;
endmodule

```

 

Q3

3) Implement 2-to-4 Decoder using conditional operator (A logic decoder has n input lines and  $2^n$  output lines. Each output line corresponds to a unique combination of the input values.)

- The design has input **A** (2 bits) and output **D** (4 bits)
- you can use the following format for the conditional operator.
- assign <output\_signal> = <condition1> ? <value1> : <condition2> ? <value2> : <default\_value>;

| A <sub>1</sub> | A <sub>0</sub> | D <sub>3</sub> | D <sub>2</sub> | D <sub>1</sub> | D <sub>0</sub> |
|----------------|----------------|----------------|----------------|----------------|----------------|
| 0              | 0              | 0              | 0              | 0              | 1              |
| 0              | 1              | 0              | 0              | 1              | 0              |
| 1              | 0              | 0              | 1              | 0              | 0              |
| 1              | 1              | 1              | 0              | 0              | 0              |

```

////////// question_3 //////////
module decoder2_4 ( output [3:0] D,
                  input  [1:0] A);
    assign D = (A==2'b00) ? 4'b0001 : (A==2'b01) ? 4'b0010 : (A==2'b10) ? 4'b0100 : 4'b1000;
endmodule

```

Q4


4) Implement an even parity generator module using assign statement. In case you don't know what a parity bit is, please check this [link](#). The design input is a bus where a reduction operator will be used to generate the even parity bit.

- The design has 1 input **A** (8 bits) and 1 output **out\_with\_parity** (9 bit) where the parity bit calculated will be inserted in the least significant bit of the output bus and the remaining bits will be the input A (Hint: use concatenation).

```

////////// question_4 //////////
module even_parity ( output [8:0] out,
                  input  [7:0] A);
    wire parity_bit;
    assign parity_bit = ^A;
    assign out = {A,parity_bit};
endmodule

```

 

Q5

5) Implement a comparator that compares 2 inputs (**A, B**) and has 3 outputs using conditional operator.

- The first output **A\_greaterthan\_B** is high only when A is greater than B
- The second output **A\_equals\_B** is high only when A equals B
- The third output **A\_lessthan\_B** is high only when A is less than B



Inputs A and B are 4-bit bus while the 3 outputs are single bits.

//////// question\_5 //////////

```
module comparator ( output A_greaterthan_B,A_lessthan_B,A_equals_B,
                    input [3:0] A,B);
    assign A_greaterthan_B = (A > B) ? 1'b1 : 1'b0;
    assign A_lessthan_B = (A < B) ? 1'b1 : 1'b0;
    assign A_equals_B = (A == B) ? 1'b1 : 1'b0;
endmodule
```

