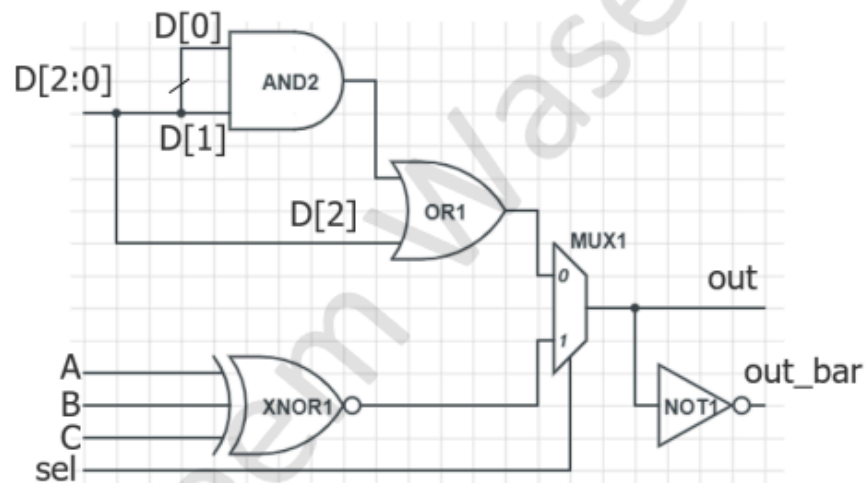


1)

- The design has 5 inputs and 2 outputs
- Randomize the stimulus in the testbench and make sure that the output is correct from the waveform



```

8 ////////////////////////////////////////////////// question_1 ///////////////////////////////////
9
10 module circuit_1 ( output out,out_bar,
11                   input [2:0] D,
12                   input A,B,C,sel);
13
14     wire w0,w1,w2;
15     and (w0,D[0],D[1]);
16     or (w1,w0,D[2]);
17     xnor (w2,A,B,C);
18     MUX2_1 e (out,w1,w2,sel);
19     not (out_bar,out);
20
21 endmodule
22
23 ////////////////////////////////// testbench ///////////////////////////////////
24
25 module circuit_1_ts ();
26 wire out,out_bar;
27 reg [2:0] D;
28 reg A,B,C,sel;
29
30 circuit_1 q (out,out_bar,D,A,B,C,sel);
31
32 initial
33 begin
34     $monitor("D=%b, A=%b, B=%b, C=%b, sel=%b -> out=%b, out_bar=%b", D, A, B, C, sel, out, out_bar);
35
36     D = 3'b000; A = 0; B = 0; C = 0; sel = 0;
37     #10;
38     D = 3'b101; A = 1; B = 0; C = 1; sel = 1;
39     #10;
40     D = 3'b011; A = 0; B = 1; C = 1; sel = 0;
41     #10;
42     D = 3'b110; A = 1; B = 1; C = 0; sel = 1;
43     #10;
44     D = 3'b111; A = 1; B = 1; C = 1; sel = 0;
45     #10;
46     $finish;
47 end
48
49 endmodule

```

VSIM 2> run -all

```

# D=000, A=0, B=0, C=0, sel=0 -> out=0, out_bar=1
# D=101, A=1, B=0, C=1, sel=1 -> out=1, out_bar=0
# D=011, A=0, B=1, C=1, sel=0 -> out=1, out_bar=0
# D=110, A=1, B=1, C=0, sel=1 -> out=1, out_bar=0
# D=111, A=1, B=1, C=1, sel=0 -> out=1, out_bar=0
# ** Note: $finish      : E:/Digital/karim_waseem/sec_2/assignment2.v(47)
# Time: 50 ns Iteration: 0 Instance: /circuit_1_ts
# 1
# Break in Module circuit_1_ts at E:/Digital/karim_waseem/sec_2/assignment2.v line 47

```

2) Design a 4-bit priority encoder, the following truth table is provided where x is 4-bit input and y is a 2-bit output. Randomize the stimulus in the testbench and add an expected result y in your testbench code and make the testbench self-checking.

x3	x2	x1	x0	y1	y0
1	X	X	X	1	1
0	1	X	X	1	0
0	0	1	X	0	1
0	0	0	X	0	0

```

module encoder_4x2 ( output [1:0] y,
                    input [3:0] x);
    assign y = (x[3]) ? 2'b11 : (x[2]) ? 2'b10 : (x[1]) ? 2'b01 : 2'b00;
endmodule

////////// testbench //////////

module encoder_4x2_ts ();

wire [1:0] y;
reg [1:0] y_expected;
reg [3:0] x;

encoder_4x2 r (y,x);

initial
begin
    repeat (10) begin
        x = $random;
        assign y_expected = (x[3]) ? 2'b11 : (x[2]) ? 2'b10 : (x[1]) ? 2'b01 : 2'b00;
        #10
        if (y!=y_expected) begin
            $display ("ERROR");
            $stop;
        end
    end
end

initial begin
    $monitor("x=%b -> y=%b , y_expected=%b", x, y, y_expected);
end

endmodule

```

```

sim:/encoder_4x2_ts/y_expected \
sim:/encoder_4x2_ts/x
VSIM 8> run -all
# x=0100 -> y=10 , y_expected=10
# x=0001 -> y=00 , y_expected=00
# x=1001 -> y=11 , y_expected=11
# x=0011 -> y=01 , y_expected=01
# x=1101 -> y=11 , y_expected=11
# x=0101 -> y=10 , y_expected=10
# x=0010 -> y=01 , y_expected=01
# x=0001 -> y=00 , y_expected=00
# x=1101 -> y=11 , y_expected=11

```

3) Design a decimal to BCD "Binary Coded Decimal" encoder has 10 input lines D0 to D9 and 4 output lines Y0 to Y3 . Below is the truth table for a decimal to BCD encoder. Output should be held LOW if none of the following input patterns is observed. Randomize the stimulus in the testbench and add an expected result y in your testbench code and make the testbench self-checking.

Input										Output			
D ₉	D ₈	D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	Y ₃	Y ₂	Y ₁	Y ₀
0	0	0	0	0	0	0	0	0	1	0	0	0	0
0	0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	0	0	0	1	0	0	0	0	1	0
0	0	0	0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	0	1	0	0	0	0	0	1	0	0
0	0	0	0	1	0	0	0	0	0	0	1	0	1
0	0	0	1	0	0	0	0	0	0	0	1	1	0
0	0	1	0	0	0	0	0	0	0	0	1	1	1
0	1	0	0	0	0	0	0	0	0	1	0	0	0
1	0	0	0	0	0	0	0	0	0	1	0	0	1

```
module BCD ( output reg [3:0] y,  
             input [9:0] D);  
    always @(*) begin  
        case (D)  
            1    : y =4'b0000;  
            2    : y =4'b0001;  
            4    : y =4'b0010;  
            8    : y =4'b0011;  
            16   : y =4'b0100;  
            32   : y =4'b0101;  
            64   : y =4'b0110;  
            128  : y =4'b0111;  
            256  : y =4'b1000;  
            512  : y =4'b1001;  
            default: y =0;  
        endcase  
    end  
endmodule
```

```

module BCD_ts ();
    wire [3:0] y;
    reg [3:0] y_expected;
    reg [9:0] D;
    integer i;

    BCD BCD_1 (y, D);

    initial begin
        D = 10'b1000000000;#10;
        D = 10'b0100000000;#10;
        D = 10'b0010000000;#10;
        D = 10'b0001000000;#10;
        D = 10'b0000100000;#10;
        D = 10'b0000010000;#10;
        D = 10'b0000001000;#10;
        D = 10'b0000000100;#10;
        D = 10'b0000000010;#10;
        D = 10'b0000000001;#10;

        for (i = 0; i < 10; i = i + 1) begin
            D = 10'b1 << i;
            y_expected = i;

            #10;

            if (y === y_expected)
                $display("PASS: D = %b -> Y = %b (Expected: %b)", D, y, y_expected);
            else
                $display("FAIL: D = %b -> Y = %b (Expected: %b)", D, y, y_expected);
        end
    end

    initial begin
        $monitor("x=%b -> y=%b , y_expected=%b", D, y, y_expected);
    end

endmodule

```

```
Transcript
# x=0000000001 -> y=0000 , y_expected=0000
# PASS: D = 0000000001 -> Y = 0000 (Expected: 0000)
# x=0000000010 -> y=0001 , y_expected=0001
# PASS: D = 0000000010 -> Y = 0001 (Expected: 0001)
# x=0000000100 -> y=0010 , y_expected=0010
# PASS: D = 0000000100 -> Y = 0010 (Expected: 0010)
# x=0000001000 -> y=0011 , y_expected=0011
# PASS: D = 0000001000 -> Y = 0011 (Expected: 0011)
# x=0000010000 -> y=0100 , y_expected=0100
# PASS: D = 0000010000 -> Y = 0100 (Expected: 0100)
# x=0000100000 -> y=0101 , y_expected=0101
# PASS: D = 0000100000 -> Y = 0101 (Expected: 0101)
# x=0001000000 -> y=0110 , y_expected=0110
# PASS: D = 0001000000 -> Y = 0110 (Expected: 0110)
# x=0010000000 -> y=0111 , y_expected=0111
# PASS: D = 0010000000 -> Y = 0111 (Expected: 0111)
# x=0100000000 -> y=1000 , y_expected=1000
# PASS: D = 0100000000 -> Y = 1000 (Expected: 1000)
# x=1000000000 -> y=1001 , y_expected=1001
# PASS: D = 1000000000 -> Y = 1001 (Expected: 1001)
```

4) Implement N-bit adder using Dataflow modeling style

- The design takes 2 inputs (A, B) and the summation is assigned to output (C) ignoring the carry.
- Parameter N has default value = 1.
- Randomize the stimulus in the testbench and add an expected result y in your testbench code and make the testbench self-checking.

```

////////// question_4 //////////

module Nbit_Adder #(parameter N = 1) ( output [N-1:0] C,
                                     input  [N-1:0] A,
                                     input  [N-1:0] B);
    assign C = A + B;
endmodule

////////// test_bench //////////

module Nbit_Adder_tb;

    parameter N = 4;
    reg  [N-1:0] A, B;
    wire [N-1:0] C;
    reg  [N-1:0] expected_C;
    integer i;

    Nbit_Adder #(4) uut (C,A,B);

    initial begin
        for (i = 0; i < 10; i = i + 1) begin
            A = $random ;
            B = $random ;
            expected_C = A + B;

            #10;

            if (C === expected_C)
                $display("PASS: A = %b, B = %b -> C = %b (Expected: %b)", A, B, C, expected_C);
            else
                $display("FAIL: A = %b, B = %b -> C = %b (Expected: %b)", A, B, C, expected_C);
        end
    end

endmodule

```

```

# PASS: A = 0100, B = 0001 -> C = 0101 (Expected: 0101)
# PASS: A = 1001, B = 0011 -> C = 1100 (Expected: 1100)
# PASS: A = 1101, B = 1101 -> C = 1010 (Expected: 1010)
# PASS: A = 0101, B = 0010 -> C = 0111 (Expected: 0111)
# PASS: A = 0001, B = 1101 -> C = 1110 (Expected: 1110)
# PASS: A = 0110, B = 1101 -> C = 0011 (Expected: 0011)
# PASS: A = 1101, B = 1100 -> C = 1001 (Expected: 1001)
# PASS: A = 1001, B = 0110 -> C = 1111 (Expected: 1111)
# PASS: A = 0101, B = 1010 -> C = 1111 (Expected: 1111)
# PASS: A = 0101, B = 0111 -> C = 1100 (Expected: 1100)


```


4) Implement N-bit adder using Dataflow modeling style

- The design takes 2 inputs (A, B) and the summation is assigned to output (C) ignoring the carry.
- Parameter N has default value = 1.
- Randomize the stimulus in the testbench and add an expected result y in your testbench code and make the testbench self-checking.

 5) Design N-bit ALU that perform the following operations

- The design has 3 inputs and 1 output
- Instantiate the half adder from the previous question to implement the addition operation of the ALU
- For the subtraction, subtract B from A "A - B"
- Parameter N has default value = 4.
- Randomize the stimulus in the testbench and add an expected result y in your testbench code and make the testbench self-checking.



Inputs		Outputs
opcode		Operation
0	0	Addition
1	0	Subtraction
0	1	OR
1	1	XOR

```

module ALU ( result,A,B,opcode);
    parameter w1 = 4;
    output reg [w1-1:0] result;
    input [w1-1:0] A,B;
    input [1:0] opcode;
    always @(*) begin
        case (opcode)
            0      : result = A + B;
            1      : result = A / B;
            2      : result = A - B;
            3      : result = A ^ B;
        endcase
    end
endmodule

```

```

module ALU_tb();

    parameter N = 4;
    reg [N-1:0] A, B;
    reg [1:0] opcode;
    wire [N-1:0] result;
    reg [N-1:0] expected_result;
    integer i;

    ALU #(N) uut (result,A,B,opcode);

    initial begin
        for (i = 0; i < 10; i = i + 1) begin
            A = $random ;
            B = $random ;
            opcode = $random ;

            case (opcode)
                2'b00: expected_result = A + B;
                2'b01: expected_result = A / B;
                2'b10: expected_result = A - B;
                2'b11: expected_result = A ^ B;
            endcase

            #10;

            if (result === expected_result)
                $display("PASS: A = %b, B = %b, Opcode = %b -> Result = %b (Expected: %b)", A, B, opcode, result, expected_result);
            else
                $display("FAIL: A = %b, B = %b, Opcode = %b -> Result = %b (Expected: %b)", A, B, opcode, result, expected_result);
            end
        end
    end
endmodule

```

```


sim:/ALU_tb/result
VSIM 12> run -all
# PASS: A = 0100, B = 0001, Opcode = 01 -> Result = 0101 (Expected: 0101)
# PASS: A = 0011, B = 1101, Opcode = 01 -> Result = 1111 (Expected: 1111)
# PASS: A = 0101, B = 0010, Opcode = 01 -> Result = 0111 (Expected: 0111)
# PASS: A = 1101, B = 0110, Opcode = 01 -> Result = 1111 (Expected: 1111)
# PASS: A = 1101, B = 1100, Opcode = 01 -> Result = 1101 (Expected: 1101)
# PASS: A = 0110, B = 0101, Opcode = 10 -> Result = 0001 (Expected: 0001)
# PASS: A = 0101, B = 0111, Opcode = 10 -> Result = 1110 (Expected: 1110)
# PASS: A = 1111, B = 0010, Opcode = 10 -> Result = 1101 (Expected: 1101)
# PASS: A = 1000, B = 0101, Opcode = 00 -> Result = 1101 (Expected: 1101)
# PASS: A = 1101, B = 1101, Opcode = 01 -> Result = 1101 (Expected: 1101)

```

6) Implement 4-bit ALU display on 7 Segment LED Display

- The design has 4 inputs: A, B, opcode, enable.
- The design has 7 outputs (a-g)
- Instantiate the N-bit ALU designed in the previous question with parameter N = 4
- ALU should execute the operation on A and B depending on the input opcode
- ALU output should be considered as the digit to be displayed on the 7 segment LED display
- Below the truth table of the 7-segment decoder
- Since we have verified the ALU and Adder, we need to make sure that the outputs a to g are correct. Write 16 directed test vectors to exercise all the below digits with enable input equals to 1 then one directed test vector to drive the enable to 0. Make the testbench self-checking.

	Input	Output						
Digit	enable	a	b	c	d	e	f	g
0	1	1	1	1	1	1	1	0
1	1	0	1	1	0	0	0	0
2	1	1	1	0	1	1	0	1
3	1	1	1	1	1	0	0	1
4	1	0	1	1	0	0	1	1
5	1	1	0	1	1	0	1	1
6	1	1	0	1	1	1	1	1
7	1	1	1	1	0	0	0	0
8	1	1	1	1	1	1	1	1
9	1	1	1	1	1	0	1	1
A	1	1	1	1	0	1	1	1
b	1	0	0	1	1	1	1	1
C	1	1	0	0	1	1	1	0
d	1	0	1	1	1	1	0	1
E	1	1	0	0	1	1	1	1
F	1	1	0	0	0	1	1	1
x	0	0	0	0	0	0	0	0

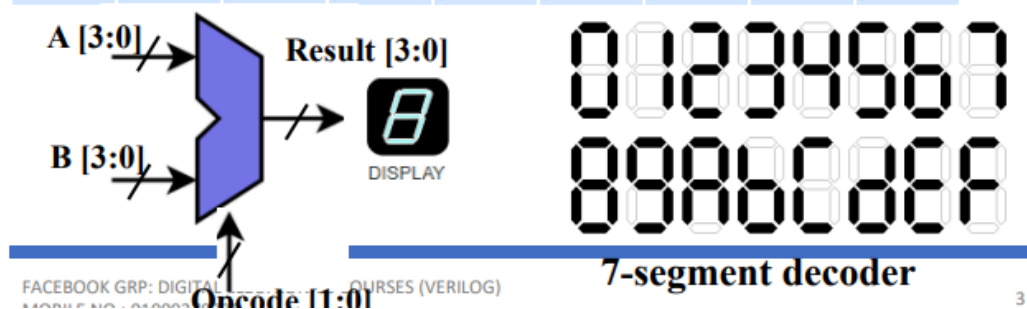

```

module Seven_Segment ([output reg [6:0] Segments],
                      input [3:0] Digit,
                      input Enable);
    always @(*) begin
        if (!Enable)
            Segments = 7'b0000000;
        else begin
            case (Digit)
                4'h0: Segments = 7'b1111110;
                4'h1: Segments = 7'b0110000;
                4'h2: Segments = 7'b1101101;
                4'h3: Segments = 7'b1111001;
                4'h4: Segments = 7'b0110011;
                4'h5: Segments = 7'b1011011;
                4'h6: Segments = 7'b1011111;
                4'h7: Segments = 7'b1110000;
                4'h8: Segments = 7'b1111111;
                4'h9: Segments = 7'b1111011;
                4'hA: Segments = 7'b1110111;
                4'hB: Segments = 7'b0011111;
                4'hC: Segments = 7'b1001110;
                4'hD: Segments = 7'b0111101;
                4'hE: Segments = 7'b1001111;
                4'hF: Segments = 7'b1000111;
                default: Segments = 7'b0000000;
            endcase
        end
    end
endmodule

```

```

module ALU_Display ( output [6:0] Segments,
                    input [3:0] A, B,
                    input [1:0] Opcode,
                    input Enable);

    parameter w3 = 4;
    wire [3:0] ALU_Result;

    ALU alu #(w3) (ALU_Result,A,B,opcode);

    SevenSegmentDecoder decoder (Segments,ALU_Result,Enable );
endmodule

```

```

module ALU_Display_tb;
    reg [3:0] A, B;
    reg [1:0] Opcode;
    reg Enable;
    wire [6:0] Segments;

    ALU_Display uut (Segments,A,B,opcode,Enable);

    initial begin
        Enable = 1;

        A = 4'h3; B = 4'h2; Opcode = 2'b00; #10;
        A = 4'h7; B = 4'h1; Opcode = 2'b01; #10;
        A = 4'hF; B = 4'hF; Opcode = 2'b10; #10;
        A = 4'h5; B = 4'hA; Opcode = 2'b11; #10;

        Enable = 0; #10;

        $stop;
    end
endmodule

```

```
# x=0000000010 -> y=0001 , y_expected=0001
# PASS: D = 0000000010 -> Y = 0001 (Expected: 0001)
# x=0000000100 -> y=0010 , y_expected=0010
# PASS: D = 0000000100 -> Y = 0010 (Expected: 0010)
# x=0000001000 -> y=0011 , y_expected=0011
# PASS: D = 0000001000 -> Y = 0011 (Expected: 0011)
# x=0000010000 -> y=0100 , y_expected=0100
# PASS: D = 0000010000 -> Y = 0100 (Expected: 0100)
# x=0000100000 -> y=0101 , y_expected=0101
# PASS: D = 0000100000 -> Y = 0101 (Expected: 0101)
# x=0001000000 -> y=0110 , y_expected=0110
# PASS: D = 0001000000 -> Y = 0110 (Expected: 0110)
# x=0010000000 -> y=0111 , y_expected=0111
# PASS: D = 0010000000 -> Y = 0111 (Expected: 0111)
# x=0100000000 -> y=1000 , y_expected=1000
# PASS: D = 0100000000 -> Y = 1000 (Expected: 1000)
# x=1000000000 -> y=1001 , y_expected=1001
# PASS: D = 1000000000 -> Y = 1001 (Expected: 1001)
```